

Solar Panel Schematic Template

In the space below, draw your solar panel configuration and provide details about each solar panel.

Be sure to:

1. Draw each solar powered circuit's arrangement (parallel/series) and the terminal it is connected to.
2. Label each panel's rated voltage and current and provide the total voltage and current for that circuit.


Team Name: Solar Panel Pals

School Name: KidWind MS

Circuit #: 1 / 3

Draw your schematic in the space below:

Three Solar Panels in Series

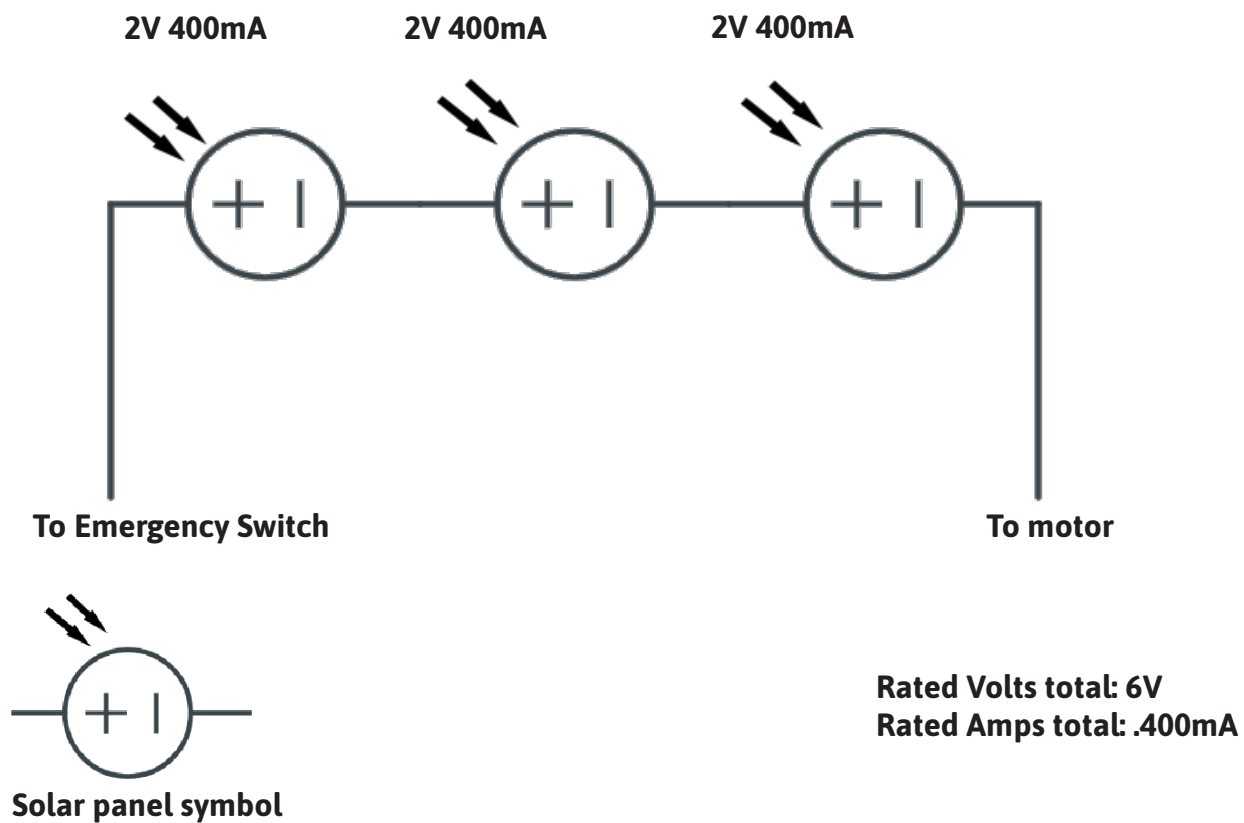

Did you:

- ☒ Provide one schematic per solar circuit
- ☒ Draw the solar panel arrangement(s)
- ☒ Label the rated voltage of each panel
- ☒ Label potential current of each panel
- ☒ Provide the total voltage and current of the circuit